

CPSC3300 – Computer Systems Organization  
Homework #3 – Boolean Algebra and Adders

Due: 3:30 PM February 8


Submit to canvas

Total 100pts


1. [2pts] Logical completeness

- a. Show that you can use only two-input NAND gates to implement each of the following two-input logic functions, and draw the used NAND gates and wiring.


i. NOR function

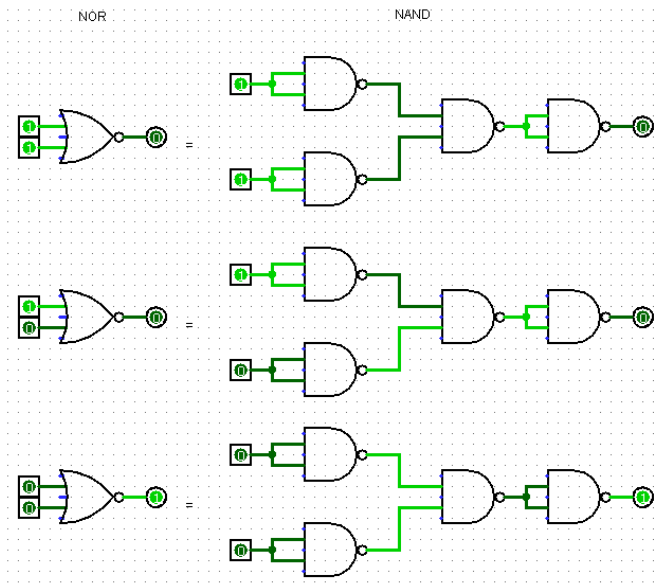


ii. XOR function

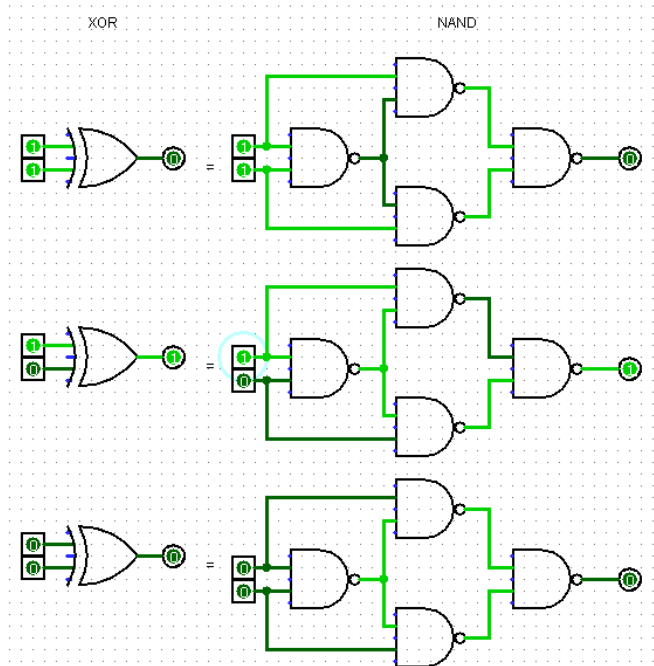

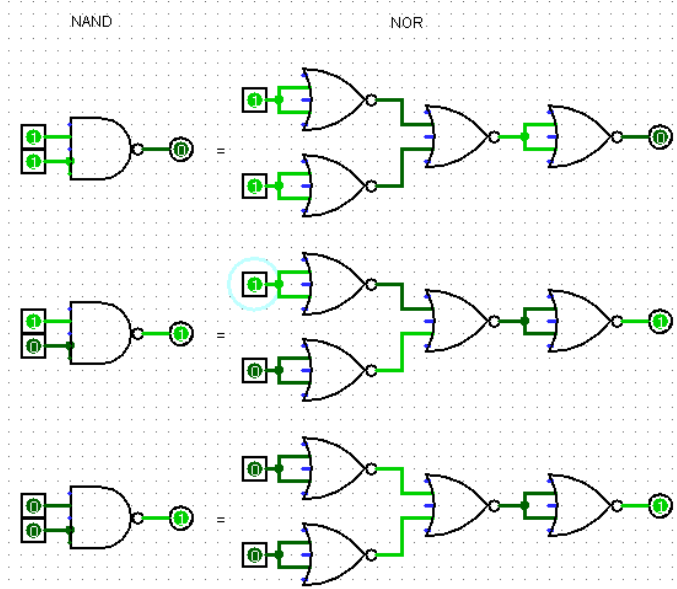
- b. Show that you can use only two-input NOR gates to implement each of the following two-input logic functions, and draw the used NOR gates and wiring.
- i. NAND function



- ii. XOR function

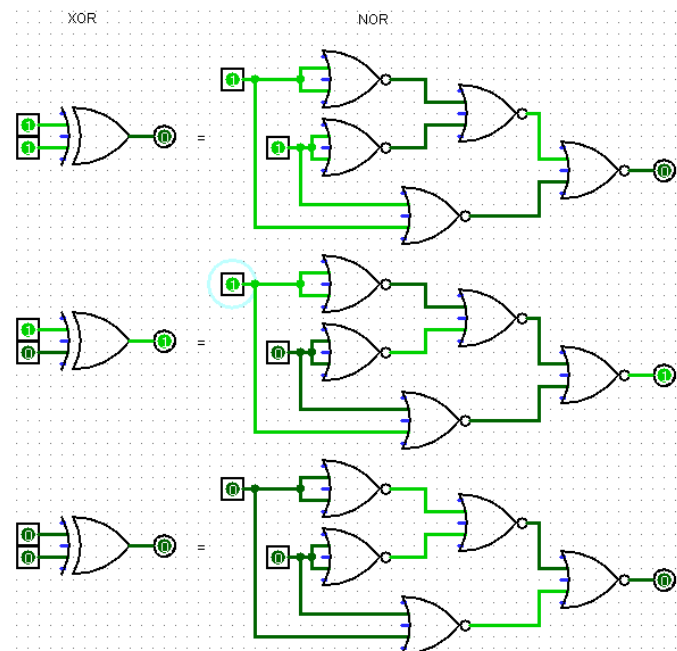

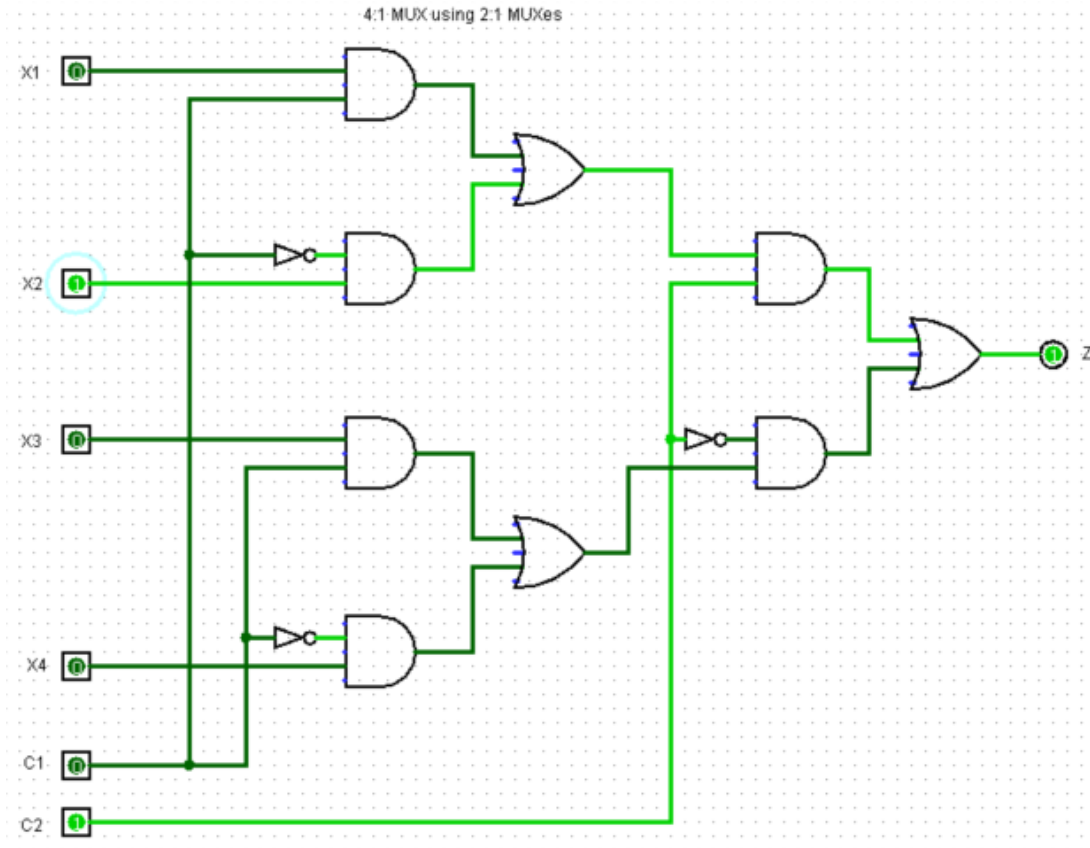2. [10pts] Show how to use 2-1 Muxes to build a 4-1 Mux. Draw the used 2-1 Muxes and the wiring, and mark the 4 inputs and 1 output for the resulting 4-1 Mux.



3. [10pts] Demonstrate by means of truth tables the validity of the following identities:

a.  $\overline{A \cdot B \cdot C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$

A	B	C	$\overline{A \cdot B \cdot C}$	$\bar{A} \cdot \bar{B} \cdot \bar{C}$
0	0	0	1	1
0	0	1	1	0
0	1	0	1	0
1	0	0	1	0
0	1	1	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	0

False

b.  $A + B \cdot C = (A + B) \cdot (A + C)$

A	B	C	$A + B \cdot C$	$(A + B) \cdot (A + C)$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
1	0	0	1	1
0	1	1	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

True

4. [20pts] Prove the identity of each of the following Boolean equations, using algebraic manipulation:

a.  $\bar{A} \cdot \bar{B} + \bar{A} \cdot B + A \cdot B = \bar{A} + B$

$$\begin{aligned} \bar{A}(\bar{B} + B) + A \cdot B &= \bar{A} + B && \text{- distributive (T3)} \\ \bar{A}(1) + A \cdot B &= \bar{A} + B && \text{- (T6)} \\ (\bar{A} + A) \cdot B &= \bar{A} + B && \text{- commutative (T1)} \\ 1 \cdot B &= \bar{A} + B && \text{- (T6)} \\ B &= B \end{aligned}$$

b.  $\bar{A} \cdot B + \bar{B} \cdot \bar{C} + A \cdot B + \bar{B} \cdot C = 1$

$$\begin{aligned} \bar{A} \cdot B + A \cdot B + \bar{B} \cdot \bar{C} + \bar{B} \cdot C &= 1 && \text{- rearrange} \\ B(\bar{A} + A) + \bar{B}(\bar{C} + C) &= 1 && \text{- distributive law (T3)} \\ B(1) + \bar{B}(1) &= 1 && \text{- (T6)} \\ B + \bar{B} &= 1 && \text{- (T6)} \\ 1 &= 1 \end{aligned}$$

5. [2pts] For the Boolean function O1 and O2, as given in the following truth table:

Input			Output	
x	y	z	O1	O2
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

- a. List the minterms for a three-variable function with variables x, y, and z.
- $\bar{x} \cdot \bar{y} \cdot \bar{z}$
  - $\bar{x} \cdot \bar{y} \cdot z$
  - $\bar{x} \cdot y \cdot \bar{z}$
  - $\bar{x} \cdot y \cdot z$
  - $x \cdot \bar{y} \cdot \bar{z}$
  - $x \cdot \bar{y} \cdot z$
  - $x \cdot y \cdot \bar{z}$
  - $x \cdot y \cdot z$
- b. Express O1 and O2 in sum-of-product algebraic form.
- $O1 = (\bar{x} \cdot \bar{y} \cdot \bar{z}) + (\bar{x} \cdot \bar{y} \cdot z) + (\bar{x} \cdot y \cdot z) + (x \cdot \bar{y} \cdot z) + (x \cdot y \cdot \bar{z})$
  - $O2 = (\bar{x} \cdot y \cdot \bar{z}) + (x \cdot \bar{y} \cdot \bar{z}) + (x \cdot y \cdot z)$
6. [20] In class, we learned the implementation for a 4-bit carry lookahead adder. We can use the same idea and extend to build a 16-bit carry lookahead adder. Denote this implementation as a one-level carry lookahead adder.
- In the textbook, Figure B.6.3 shows a two-level implementation of a 16-bit carry lookahead adder. This adder uses 4-bit carry lookahead adders at the lower level, and uses a carry lookahead unit at the higher level.
- Compare these two implementations and provide your explanation why the two-level implementation could be preferred.

The two-level implementation is generally more efficient because it requires the signals which anticipate a carry to travel through fewer gates. The reason that this is important is because by definition, a CLA “looks ahead” to see if a carry will be occurring, and the sooner this can be confirmed/denied, the faster the operation of the adder will be.